



Co-funded by the  
Erasmus+ Programme  
of the European Union





Remote Lab For Engineering Project  
Erasmus+ Program


## Raspberry Pi -Take Home Lab

### Lab Experiment # 3

Raspberry Pi- Digital Inputs

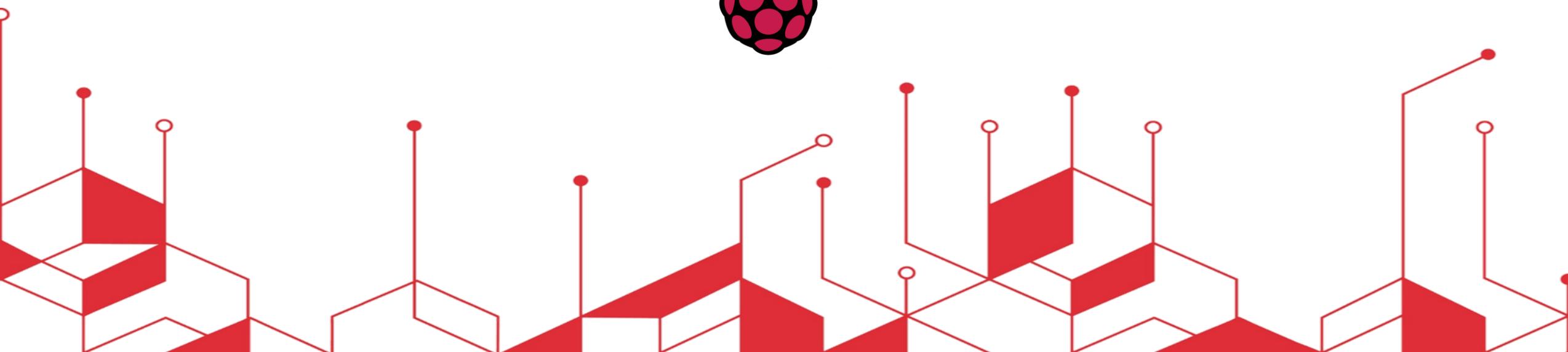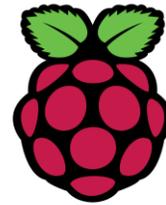

# Digital Inputs

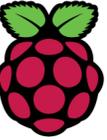


Digital inputs (DI) are signals or data received by a system in a digital (binary) format, typically as a high (1) or low (0) voltage level. They are used to detect the state of external devices or switches, such as:

- Button presses (ON/OFF).
- Status signals from sensors (e.g., presence detection, limit switches).
- Logic-level signals from other systems or microcontrollers.


## Voltage Levels:

High state (1) and Low state (0) depend on the voltage threshold, which varies by system (e.g., 0-5V, 0-3.3V).


# Push Button

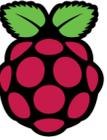

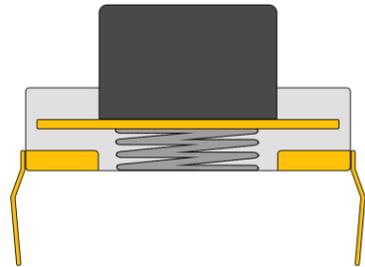
A small button or knob that when pushed connects all terminals together.



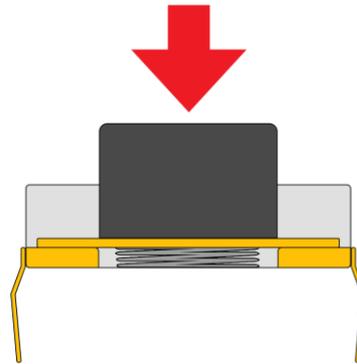
Button not pushed  
(i.e., released)  
a and c are not connected to  
b and d



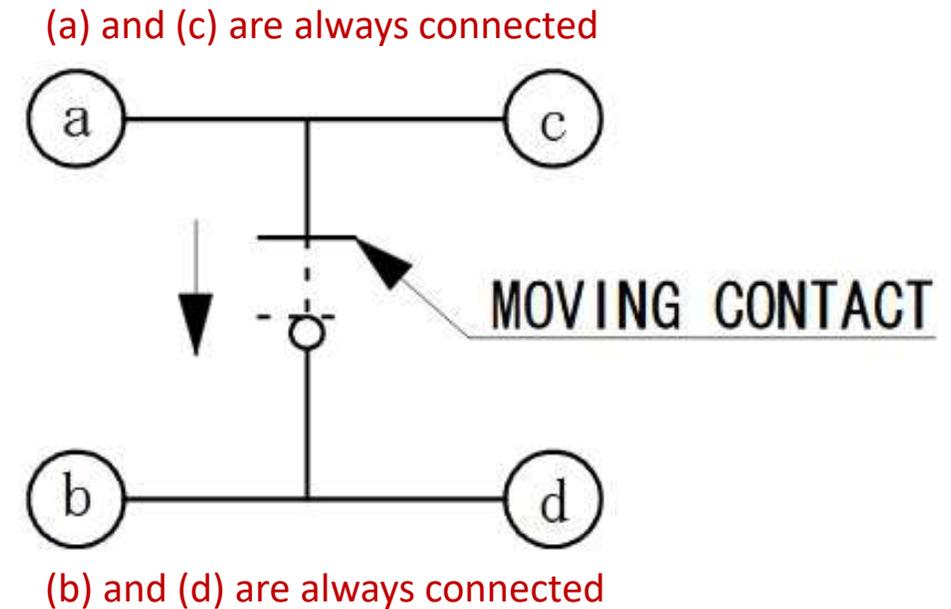Button pushed  
(i.e., pressed)  
a and c are connected to  
b and d




# Pushbutton & LED

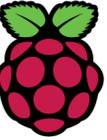


❖ Try to build the shown circuit


## Schematic Diagram

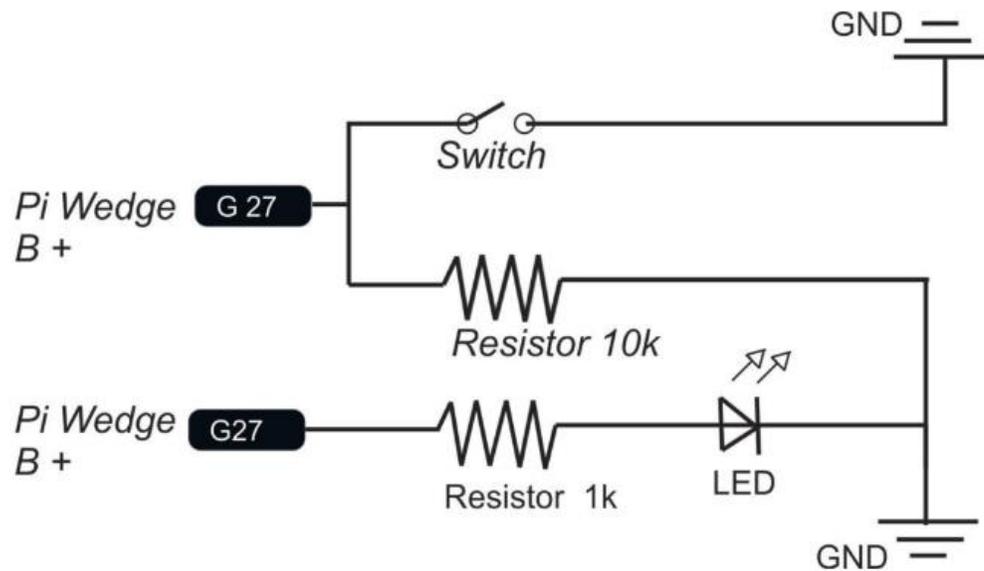

## Wiring Diagram

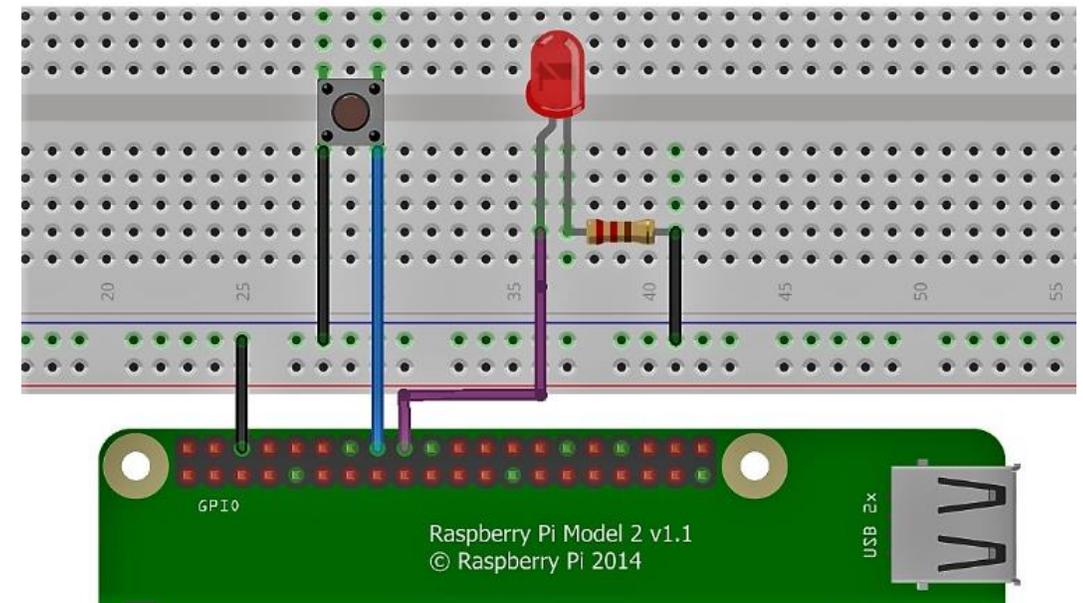

# Code


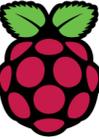


```
import RPi.GPIO as GPIO
import time


GPIO.setmode(GPIO.BCM)

GPIO.setup(23, GPIO.IN, pull_up_down=GPIO.PUD_UP)#Button to GPIO23
GPIO.setup(24, GPIO.OUT) #LED to GPIO24

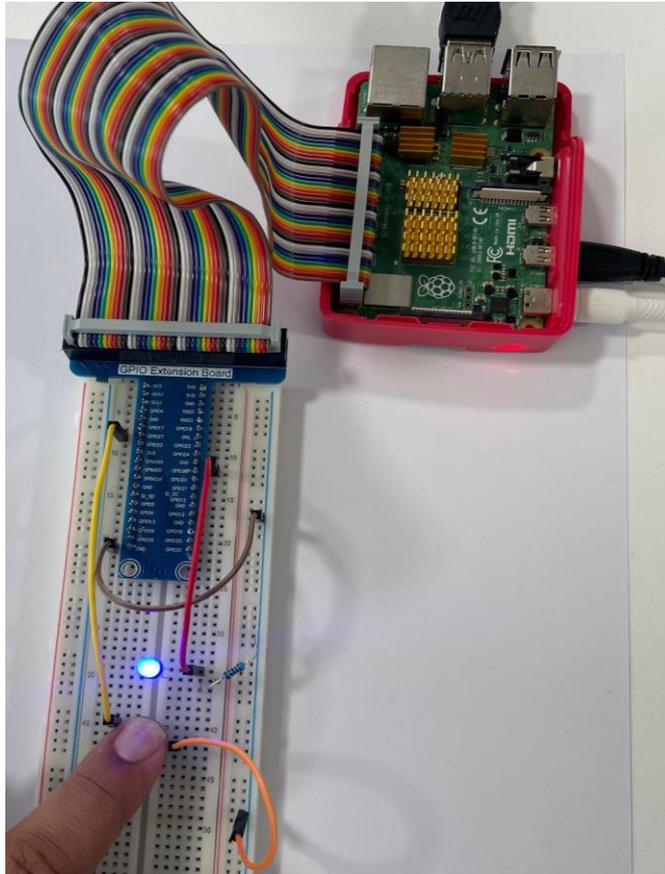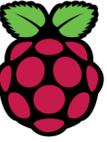try:
    while True:
        button_state = GPIO.input(23)
        if button_state == False:
            GPIO.output(24, True)
            print('Button Pressed...')
            time.sleep(0.2)
        else:
            GPIO.output(24, False)
except:
    GPIO.cleanup()
```




**Push button is pressed**

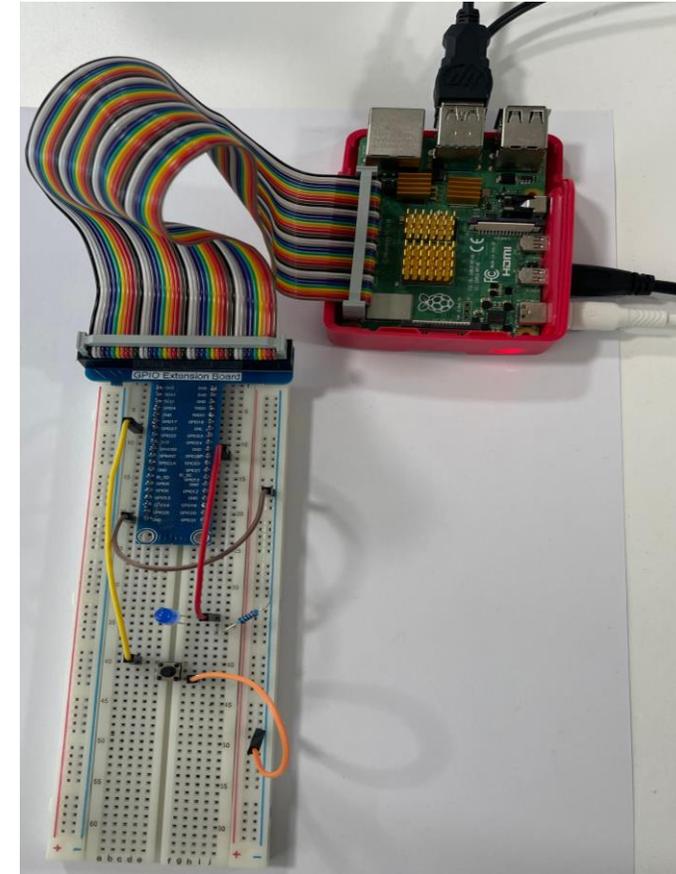

**Push button is released**


# Practice 1- Combination of two LEDs

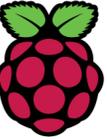

Build a circuit where the push button is used to turn a green LED off and a red LED on

- If button is not pressed,  
green ON, red OFF
- When button is pressed,  
green OFF, red ON

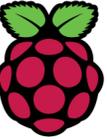
## Practice 2 – Two push buttons in series



Build a circuit where two push buttons in series are used to turn the LED on:

- When one of the buttons is not pressed (or both), the LED is **OFF**
- When both buttons are pressed at the same time, the LED is **ON**

# Take-home Task

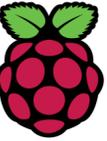

Build a circuit where push button is used to turn a relay **on** and **off**.

